 


Behavioral Modeling for SoC Simulation

Bridging Analog and Firmware Demands


Rainer Findenig
Infineon Technologies






"Set x to achieve optimized y !"

Analog Abstractions

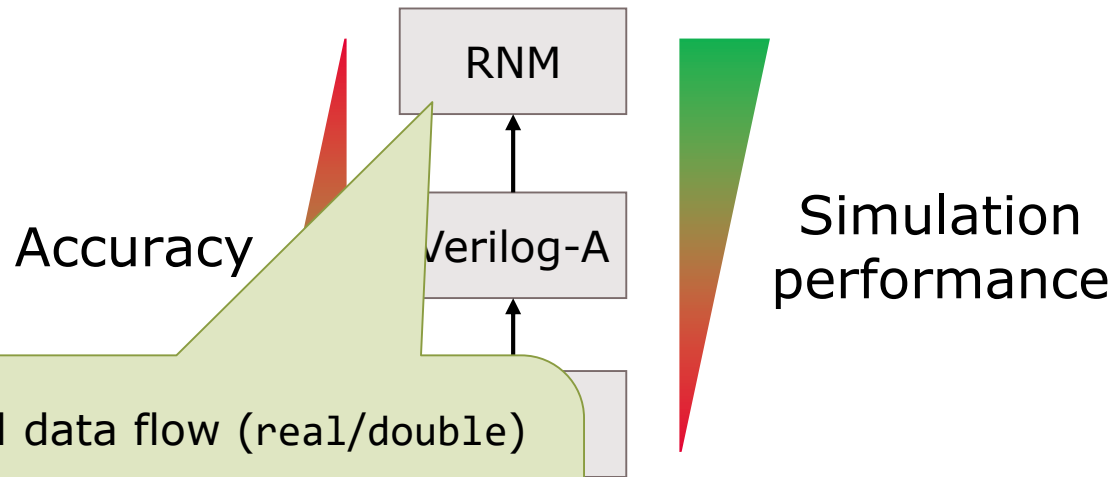


- Unidirectional data flow (real/double)
- Continuous value, discrete time
- No analog solver required
- Event-driven simulator


Event-Driven Simulation

 




Real-Number Modeling

 

 
```
always @(i, gain)
    o = i * gain;
```



Real-Number Modeling

   


Representing Analog Signals

 


piecewise constant

$$x(t) = a$$

 

piecewise linear

$$x(t) = a + b(t - t_0)$$

 


piecewise exponential

$$x(t) = a_0 + \sum_i a_i e^{-p_i(t-t_0)}$$


B. C. Lim, J. E. Jang, J. Mao, J. Kim, and M. Horowitz, "Digital Analog Design: Enabling Mixed-Signal System Validation," *IEEE Design Test*, vol. 32, no. 1, pp. 44–52, Feb. 2015.

J. E. Jang, M. J. Park, D. Lee, and J. Kim, "True event-driven simulation of analog/mixed-signal behaviors in SystemVerilog: A decision-feedback equalizing (DFE) receiver example," in *Proceedings of the IEEE 2012 Custom Integrated Circuits Conference*, 2012, pp. 1–4.



Modeling an Analog PLL

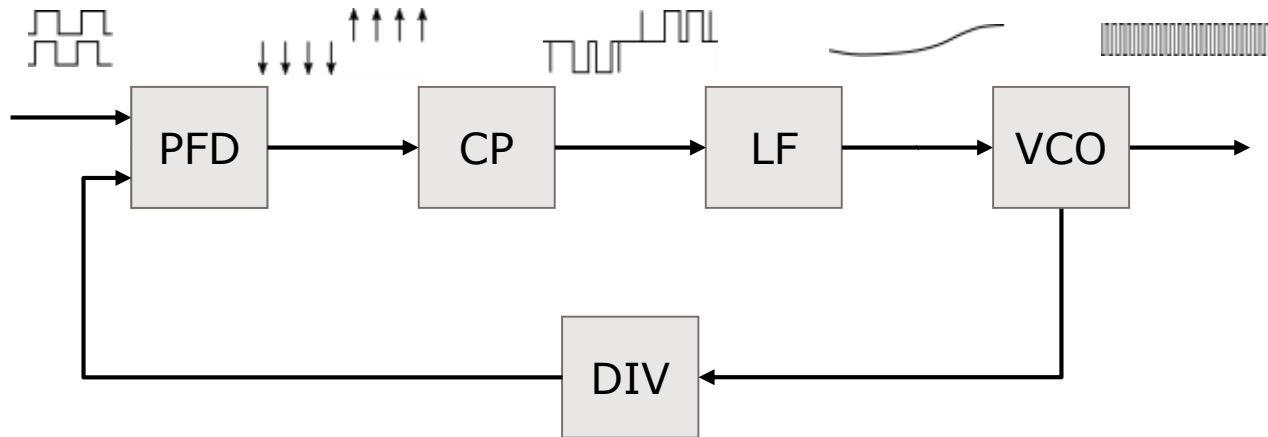



Piecewise Constant

 


Piecewise Constant

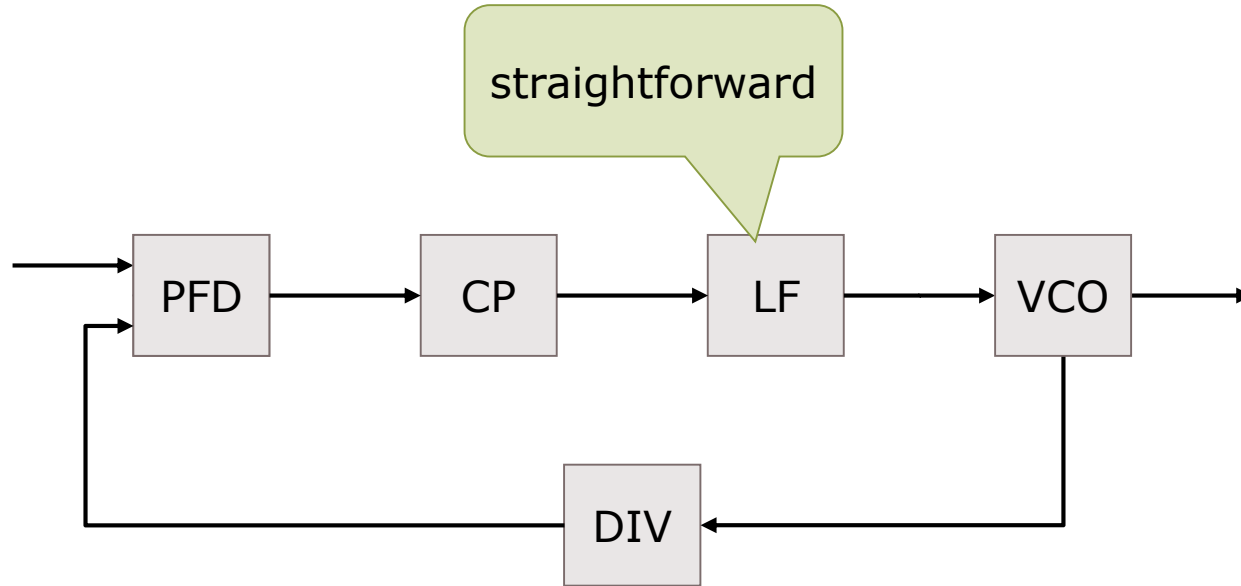 


Piecewise Constant

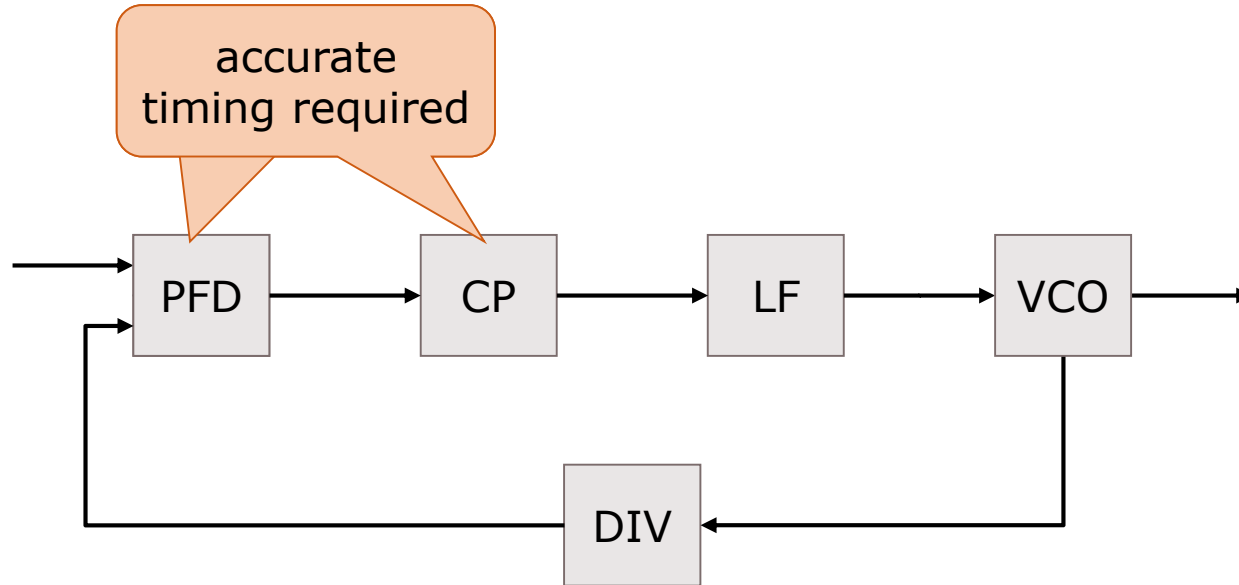 

Piecewise Constant


 


 time-continuous/value-discrete
transformed to
time-discrete/value-continuous





M. H. Perrott, "Fast and accurate behavioral simulation of fractional-N frequency synthesizers and other PLL/DLL circuits," in *Proceedings 2002 Design Automation Conference*, 2002, pp. 498–503.


Piecewise Constant

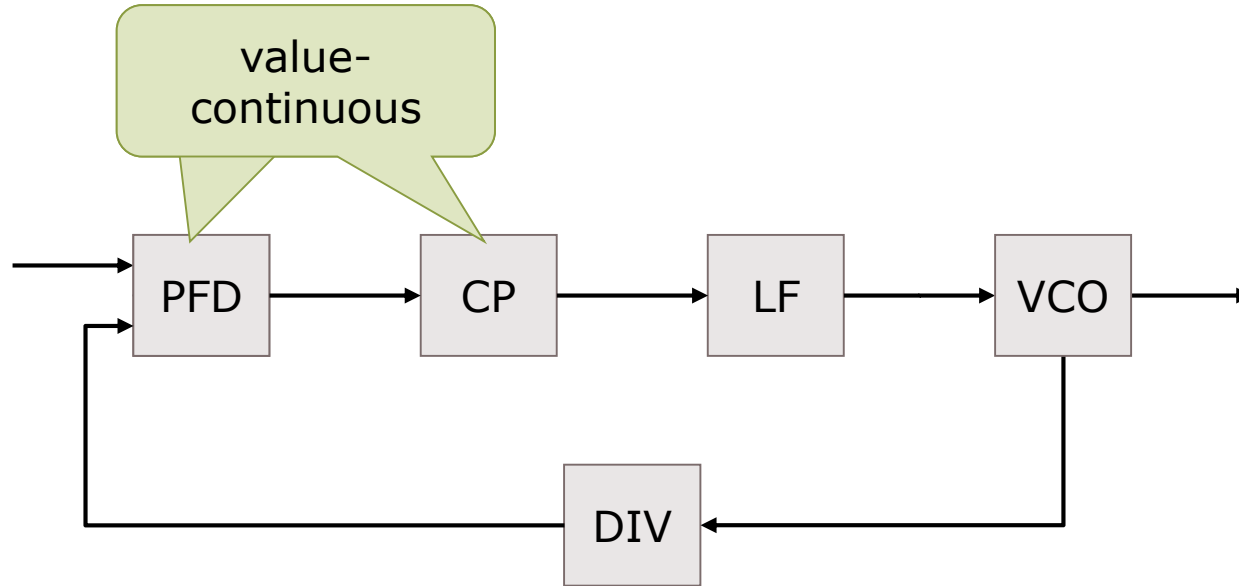 

Piecewise Constant

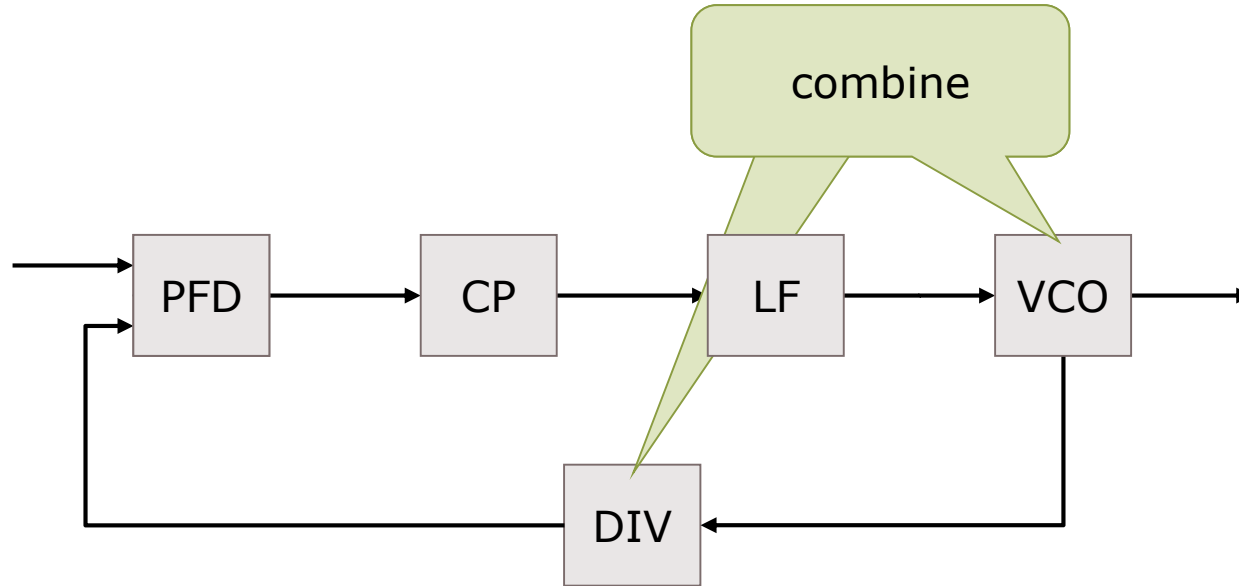 


Piecewise Constant


 


- + Easy to model
- + Structure readily obvious
- + Real-number datatypes
- $\geq 10x$ oversampling



Piecewise Linear

 



Piecewise Linear

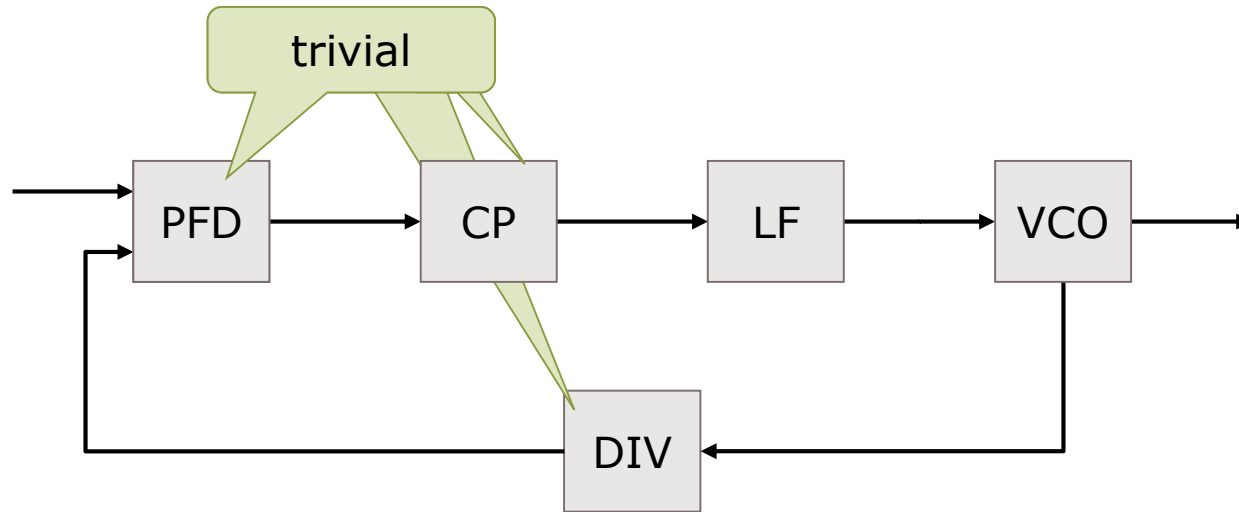 


Piecewise Linear

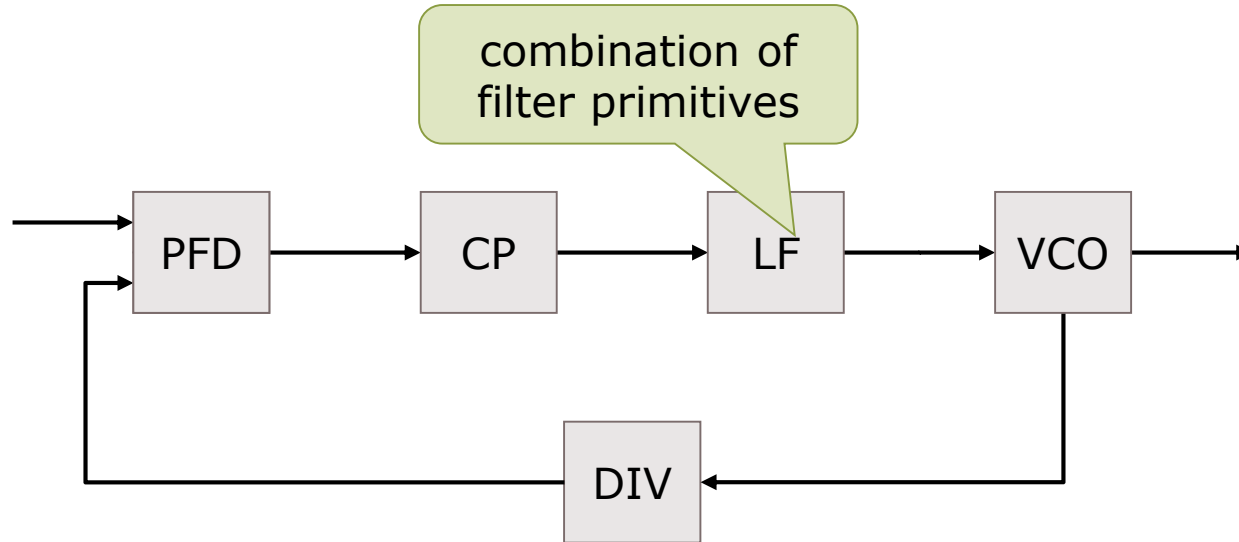 


Piecewise Linear

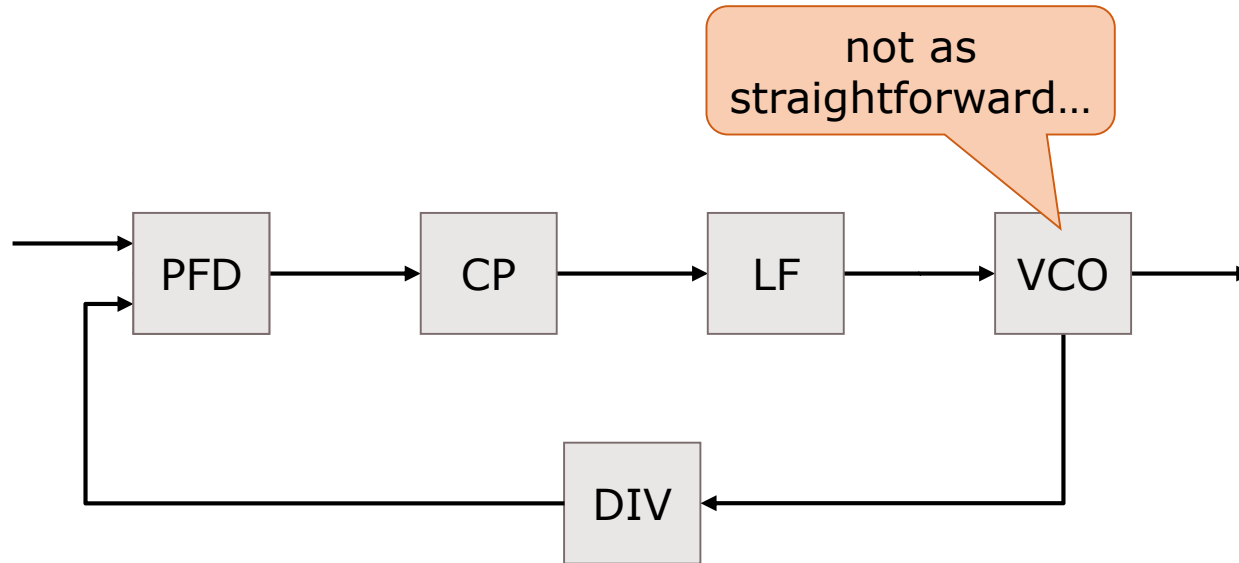 

Piecewise Linear

 


- › VCO's output is highly nonlinear...

 


B. C. Lim, J. E. Jang, J. Mao, J. Kim and M. Horowitz, "Digital Analog Design: Enabling Mixed-Signal System Validation," *IEEE Design & Test*, vol. 32, no. 1, pp. 44-52, Feb. 2015.

Piecewise Linear


 


 › ...but not when considering the frequency/phase domain!




B. C. Lim, J. E. Jang, J. Mao, J. Kim and M. Horowitz, "Digital Analog Design: Enabling Mixed-Signal System Validation," *IEEE Design & Test*, vol. 32, no. 1, pp. 44-52, Feb. 2015.

Piecewise Linear

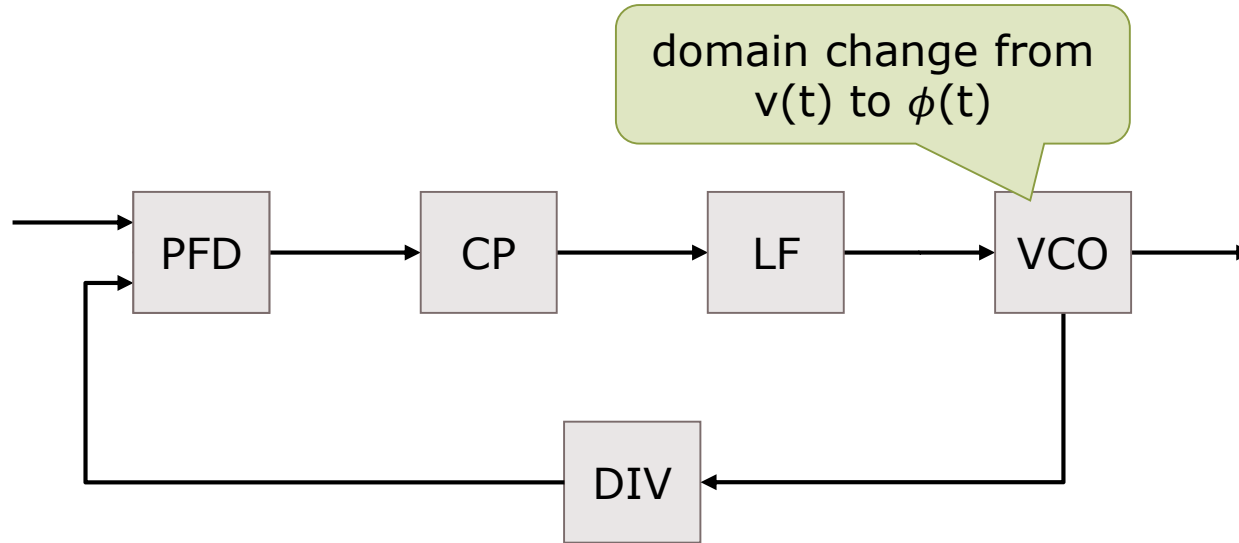 


Piecewise Linear


 


- + Easy to model
- + Close to original structure
- + Significantly faster
- Three-valued datatypes
- More samples than necessary



Piecewise Exponential

 



Piecewise Exponential

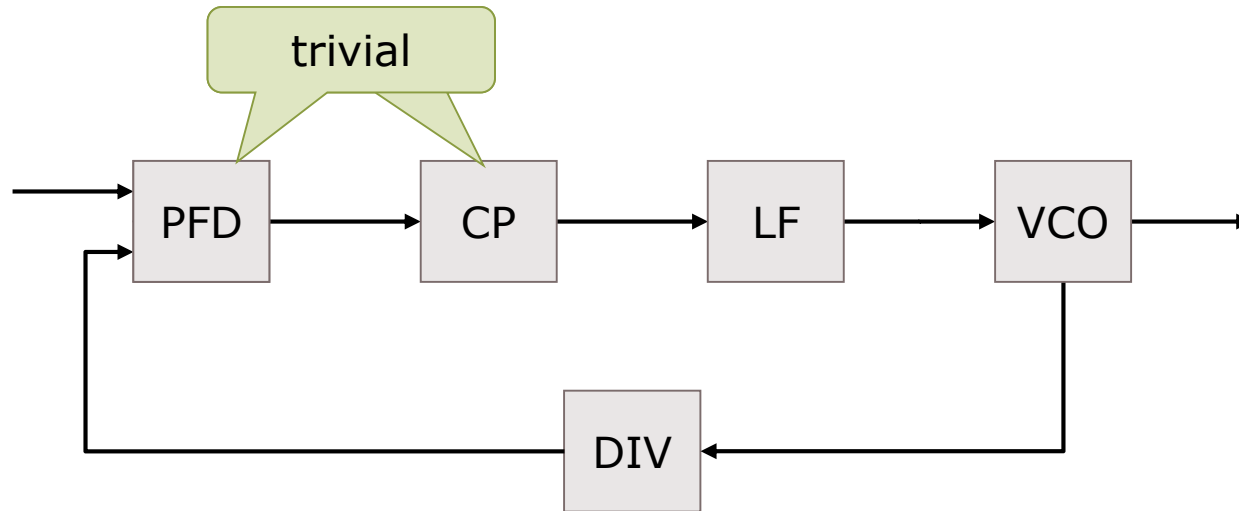 

Piecewise Exponential

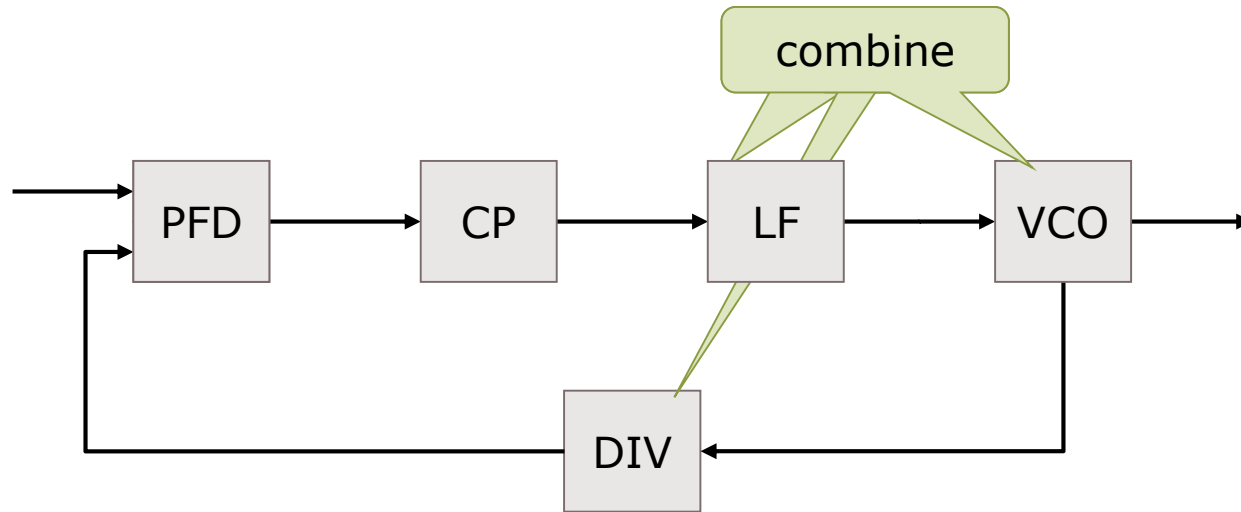 

Piecewise Exponential

  

$$I_1(s) = \dots$$

$$I_2(s) = \dots$$

$$V_2(s) = \dots = V_{\text{fine}}$$

$$I_{\text{in}}(s) = \sum_i I_i(s)$$



$$\Phi(s) = 2\pi \frac{f_0 - k_{\text{vco}} v_{\text{fine}}(0)}{s^2} + 2\pi k_{\text{vco}} \frac{V_{\text{fine}}(s)}{s} + \frac{\phi_0}{s}$$



$$\phi(t) = f(v_0, \phi_0, i_{\text{in}}, f_0, k_{\text{vco}}, t)$$


M. V. Paemel, "Analysis of a charge-pump PLL: a new model," *IEEE Transactions on Communications*, vol. 42, no. 7, pp. 2490–2498, Jul. 1994.

Piecewise Exponential

  


M. H. Perrott, M. D. Trott, and C. G. Sodini, "A modeling approach for Σ - Δ fractional-N frequency synthesizers allowing straightforward noise analysis," *IEEE Journal of Solid-State Circuits*, vol. 37, no. 8, pp. 1028–1038, Aug. 2002.

Piecewise Exponential

 


- + Minimal number of samples
- + Accurate (no approximation in LF)
- + Even faster
- Many-valued datatypes
- Equation set needs to be solved
- Numerical solution
- Loop filter and VCO not separable


Summary

 

Summary

 


Summary

 


Summary

 
complex data type:
more information, fewer events



piecewise constant

 

piecewise linear


 


piecewise exponential

calculation complexity vs.
number of events

Outlook

  - › Similar results achieved for a switch-mode power supply system
 - Digital IC + external analog components
- › Representing continuous-wave signals



- › Mapping functional models to FPGA/GPU



Part of your life. Part of tomorrow.

